

Zener Diode as Voltage Regulation.

Aim:

To simulate the line and load regulation operation using zener diode.

Apparatus Required:

Laptop with proteus Software.


Theory:

A heavily doped pn Junction diode is called zener diode. Due to heavily doped nature zener diode works under forward bias and reverse bias condition.

Zener diode under reverse bias condition is used as a voltage regulation. Even if the input voltage changes the output is constant. This is called line regulation.

If the load resistance changes the output voltage is constant this is called load regulation.

Circuit diagram:

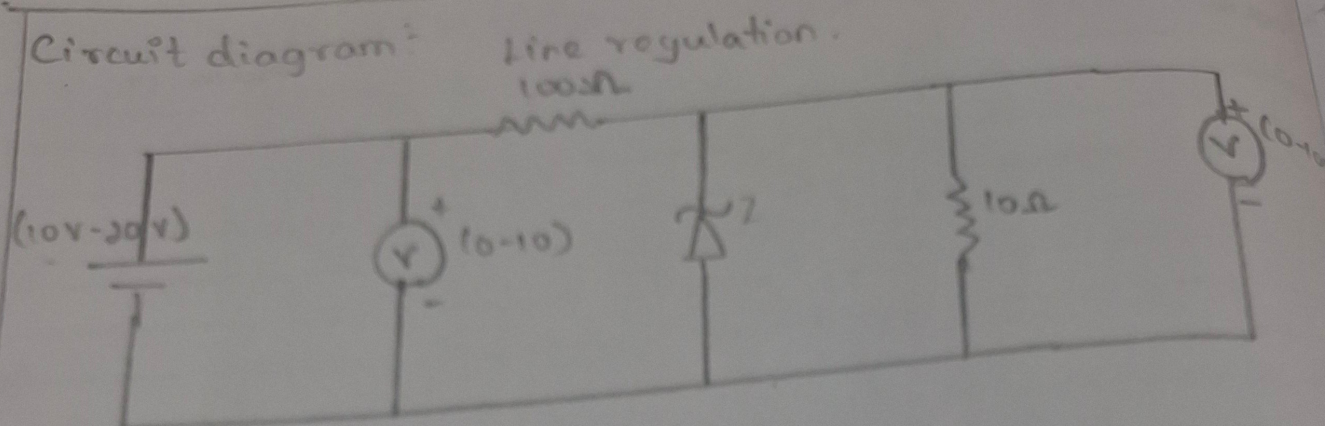

Tabulation

S.No	Input voltage	output voltage V_o (V)
1	+ 12.0	+ 5.14
2	+ 13.0	+ 5.16
3	+ 14.0	+ 5.17
4	+ 15.0	+ 5.17
5	+ 16.0	+ 5.18
6	+ 17.0	+ 5.19

Model Graph:

output voltage V_o (V)


Input voltage (V)

procedure :

1. Drag The required components from The proteus Library.
2. connect The components (required) as per circuit diagram.
3. For The $\ast$ line regulation vary The input voltage and not The output voltages in the tabulation. Draw the graph between input and output voltages.
- A. For load regulation vary the load regulation. Vary the load resistance and note The output voltage in tabulations. Draw The graph between load resistance and outputs voltage.

Circuit Diagram:

Load Regulation

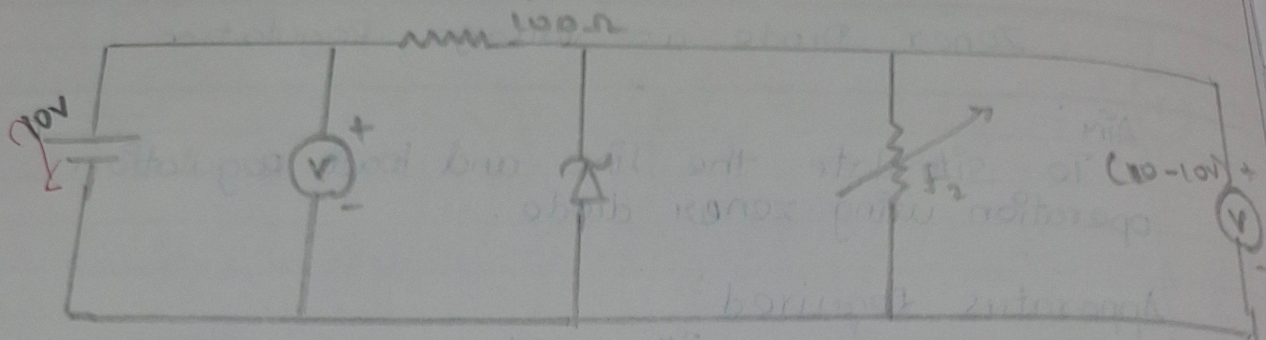

Tabulation:



S.NO	Load Resistance $R_2 (\Omega)$	Output Voltage $V_0 (V)$
1	100 Ω	5.19 V
2	200 Ω	5.20 V
3	300 Ω	5.20 V
4	400 Ω	5.20 V
5	500 Ω	5.20 V
6	600 Ω	5.21 V


Model diagram:

output
Voltage
 $V_0 (V)$

Load Resistance $R_2 (\Omega)$

output:

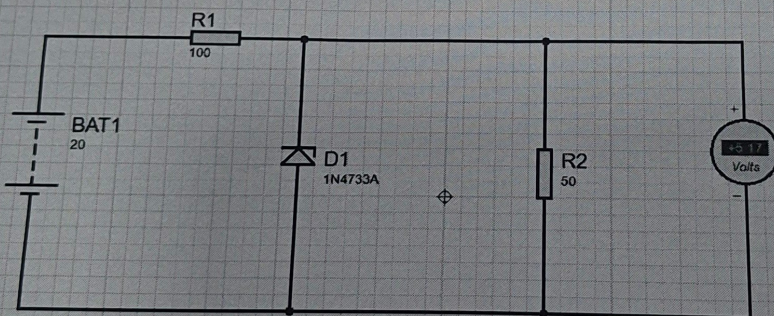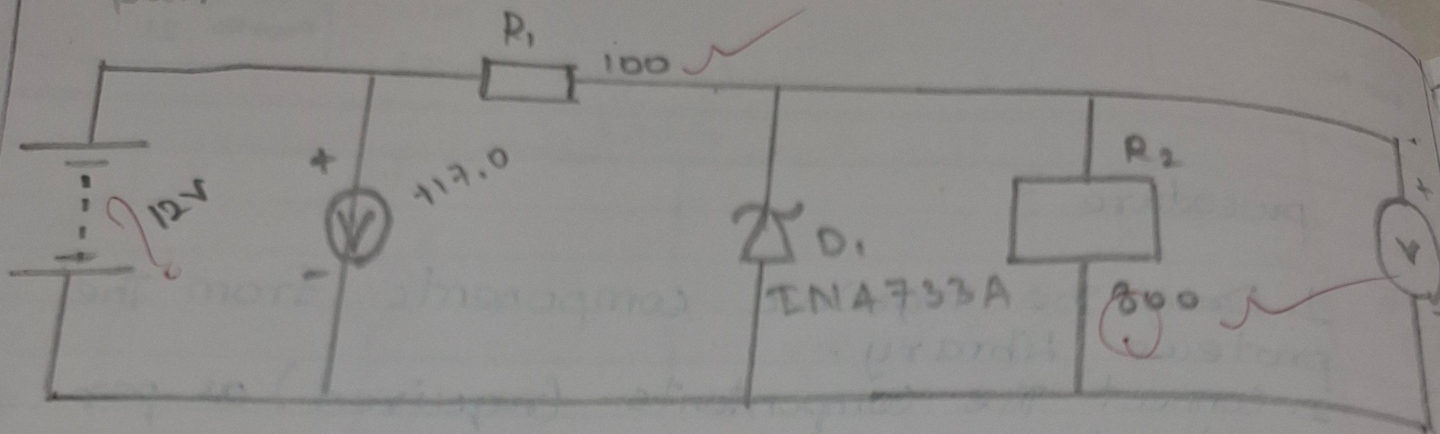

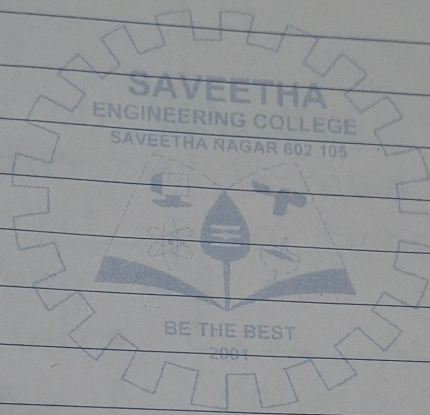

Result:

Thus simulation of The line and load regulation operation of Zener diode is successfully completed.